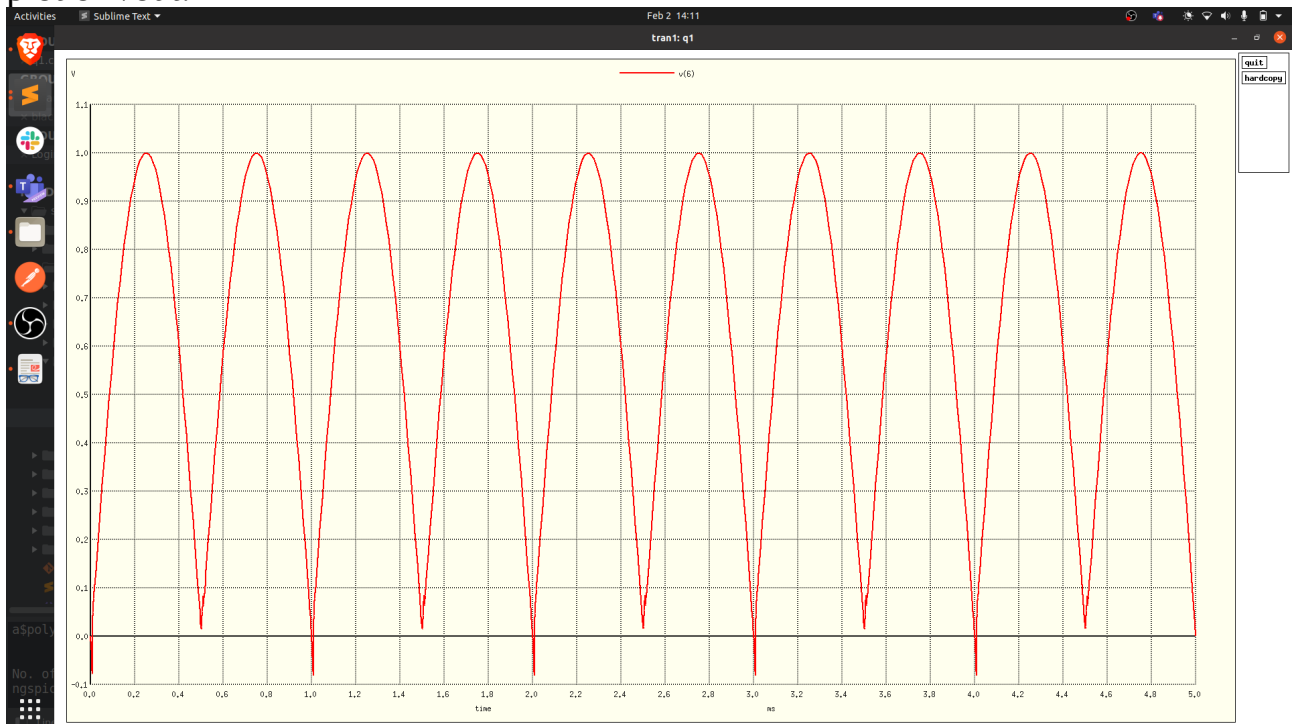


19D070052, 236 quiz1 report


Q1.

netlist in submission

plot of vout:




plot of vout vs vin:

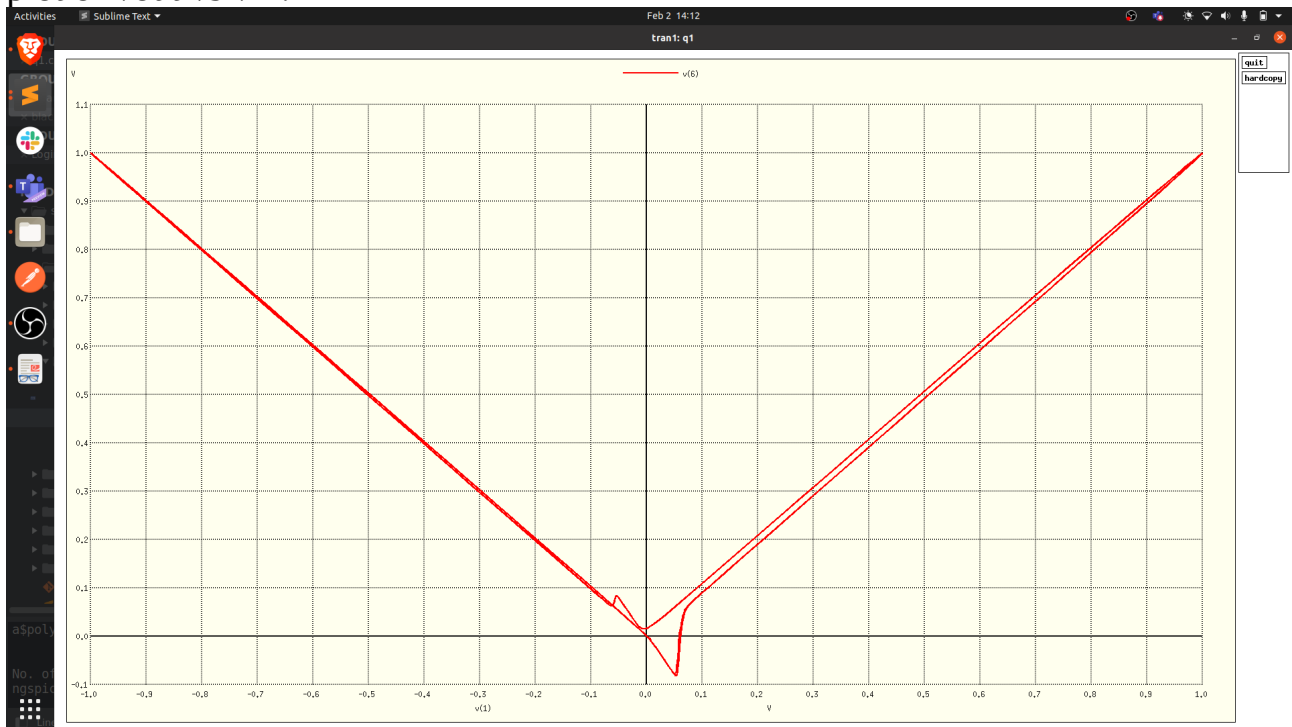

we see that  $v_{out}/v_{in}$  ratio is exactly 1 for high  $v_{in} \Rightarrow$  there is no diode drop, unlike full wave rectifier. However, there is some non-linearity close to zero  $\Rightarrow$  the new rectifier retains some voltage and hence  $v_{out}$  isn't 0 when  $v_{in}$  is 0.

Q2.

plot of IV characteristic:

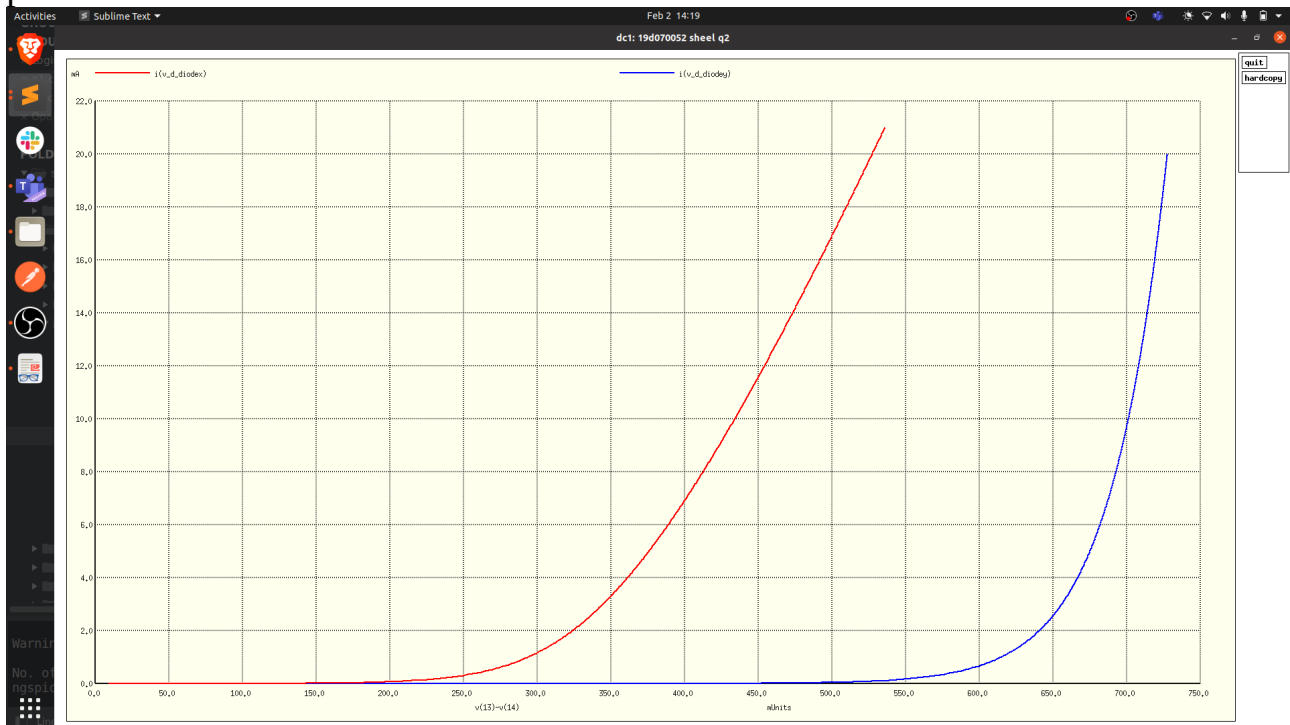

values derived using the method of lab1:

(1 is diode X, 2 is Y, eta is ideality\_factor, vd is forward voltage, isat is reverse saturation current, piv is peak inverse voltage)

eta1 = 1.310782e+00

eta2 = 1.447548e+00

vd1 = 0.293

vd2 = 0.616

isat1 = 2.00004e-07

isat2 = -8.14376e-11

piv1 = -76V


piv2 = -1000V

Plots used were I vs V, ln(I) vs V, I vs V(with line at 1mA), I vs V (with large negative values for V). Since code is similar, only one has been included in submission.

Germanium diode has lower forward drop and hence can be used in rectifiers where  $v_{out}$  is needed to be as high as possible.


Q3.

C\_dut vs |V\_dut|:

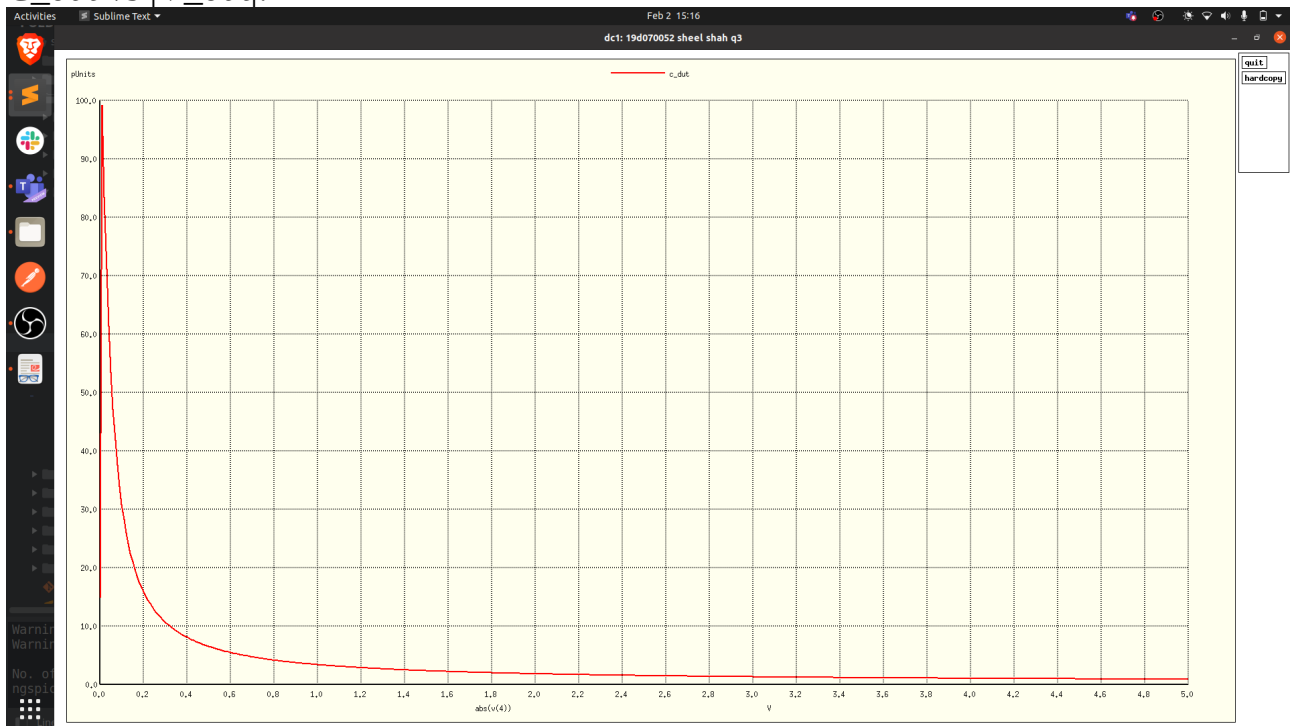

we see that the curve is like that of  $1/x^2$  and hence  $1/c_{dut}^2$  should be linear. This is also intuitive because  $c$  should decrease as the reverse potential is increased.

$1/C^2$  vs  $V_{\text{dut}}$ :

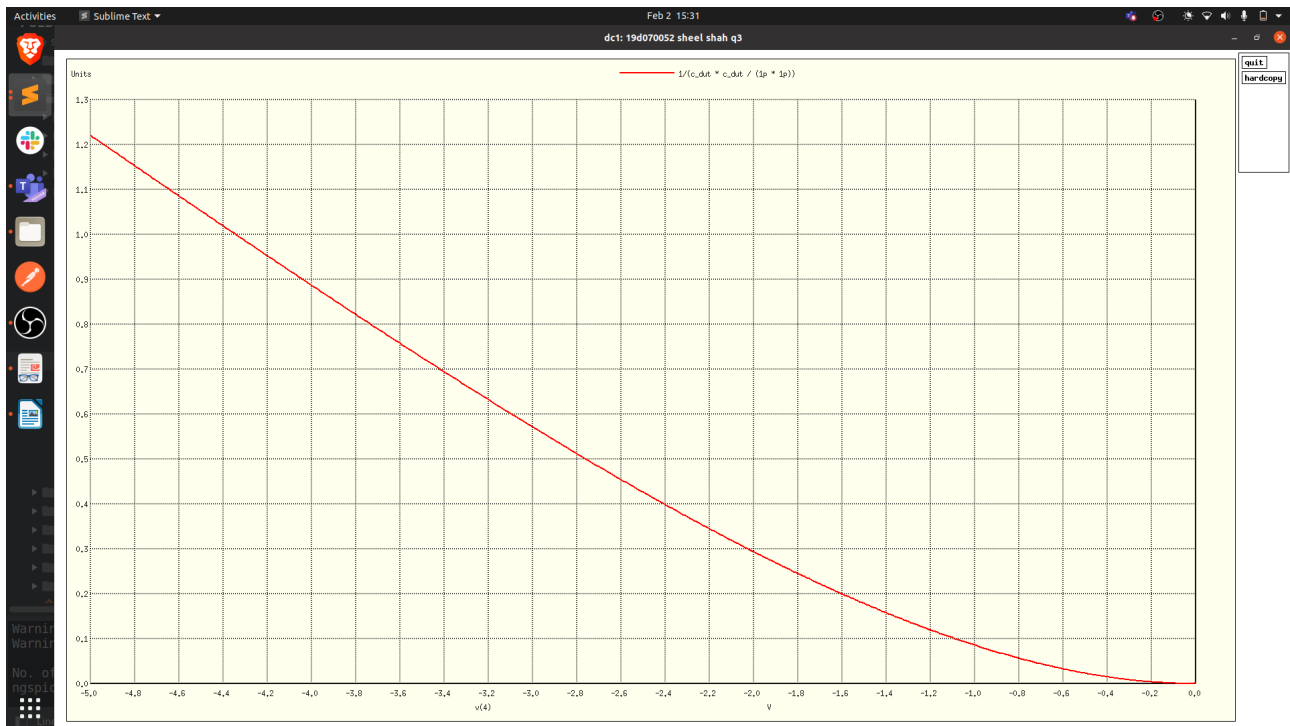

we see that it is linear

the slope is -0.32.

Comparing with equation gives  $N_d = 3.8 * 10^{23}$  atoms/cm<sup>3</sup>

Extrapolating linear region gives  $V_{\text{bi}} = -1.21$  V