

# EE236: Experiment 4

Sheel F. Shah, 19D070052

February 19, 2022

## Overview of the experiment

### 0.1 Aim of the experiment

The aim of this experiment was to understand the workings of solar cells as temperature varies. We also look at the effect of  $R_s$  and  $R_{sh}$  on the characteristics of the solar cell.

### 0.2 Report Pattern

Instead of following the template, I have split the report into sections based on the questions/simulations. Each section is based on one question/simulation, and all associated details are in that section only.

# 1 IV characteristics of solar cell

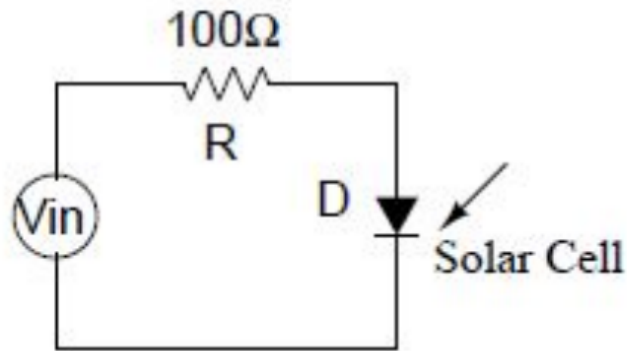


Figure 1: Circuit used

Netlist used:

```
19D070052 Sheel Shah Solar IV
.include Solar_Cell.txt

v_dc 1 0

r1 1 21 100
x1 21 31 solar_cell IL_val = 0e-3
v_dummy1 31 0 0
.dc v_dc 0.01 2 0.01 temp 35 75 10

* start control
.control
set color0 = rgb:f/f/e
set color1 = rgb:1/1/1

run

plot i(v_dummy1) vs v(21)-v(31), 1m vs v(21)-v(31), 5m vs v(21)-v(31)
```

```

* end control
.endc

.end

```

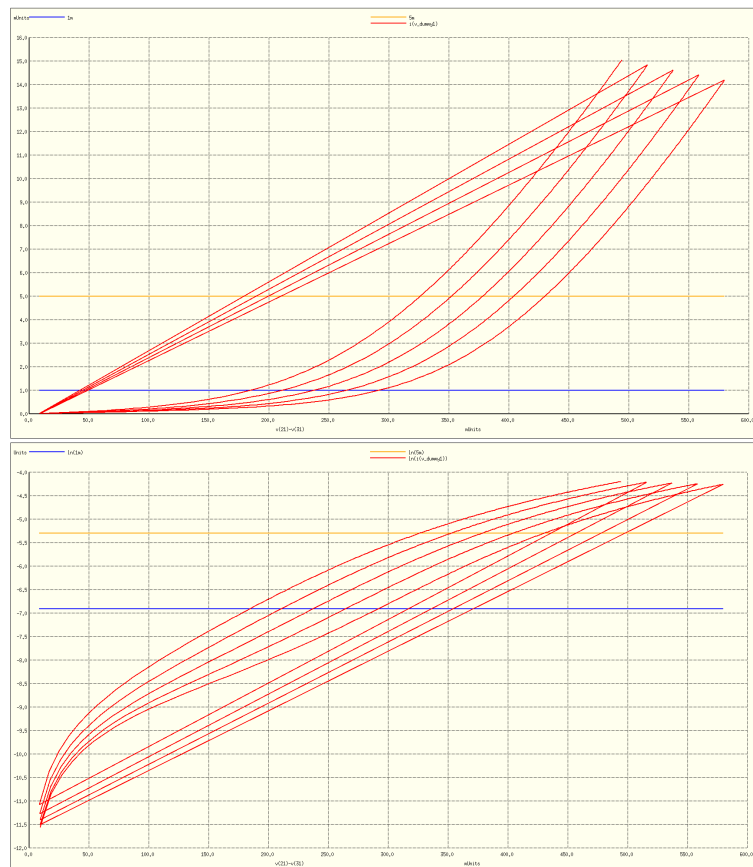


Figure 2: IV Characteristics and  $\ln I$  vs  $V$  plot

Ideality factor calculation:

Step 1 was to calculate the slope of  $\ln I$  vs  $V$  plot.

Step 2 was to calculate  $\eta = 1/(\text{slope} * V_T)$

Temp.	$V_d(I_d = 1mA)$	$V_d(I_d = 2mA)$	$V_d(I_d = 5mA)$	$\eta(I_d = 1mA)$	$\eta(I_d = 5mA)$
35	0.29	0.35	0.43	2.98	4.42
45	0.26	0.32	0.40	2.91	4.29
55	0.24	0.29	0.38	2.86	4.11
65	0.21	0.27	0.35	2.79	4.02
75	0.18	0.24	0.33	2.64	3.88

Table 1: Table 1

## 2 $I_{SC}$ and $V_{OC}$ measurement, and fill factor calculation

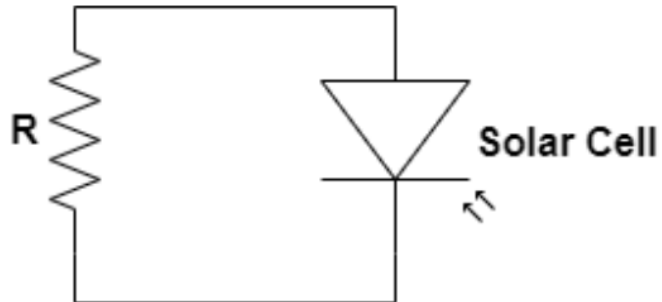


Figure 3: Circuit used

```
19D070052 Sheel Shah Solar IV
.include Solar_Cell.txt

r2 0 22 100
x2 22 32 solar_cell IL_val = 8e-3
v_dummy2 0 32 0

* start control
.control
set color0 = rgb:f/f/e
set color1 = rgb:1/1/1

run

dc r2 1 500 1 temp 35 75 10
let i1 = i(v_dummy2)
let v1 = v(22)-v(32)
let p1 = i1*v1
```

```

plot dc1.i1 vs dc1.v1
plot dc1.p1 vs dc1.v1

** values: 35 to 75
** i_sc = 7.89m, 7.88m, 7.86m, 7.82m, 7.76m
** v_oc = 392m, 368m, 343m, 319m, 294m
** p_mp = 1.60m, 1.43m, 1.28m, 1.13m, 0.98m
** ff = 0.517, 0.493, 0.475, 0.453, 0.430
* end control
.endc

.end

```

All measured values are mentioned in the code  
 $I_{sc}$ ,  $V_{oc}$  and fill factor, all decrease linearly with temperature

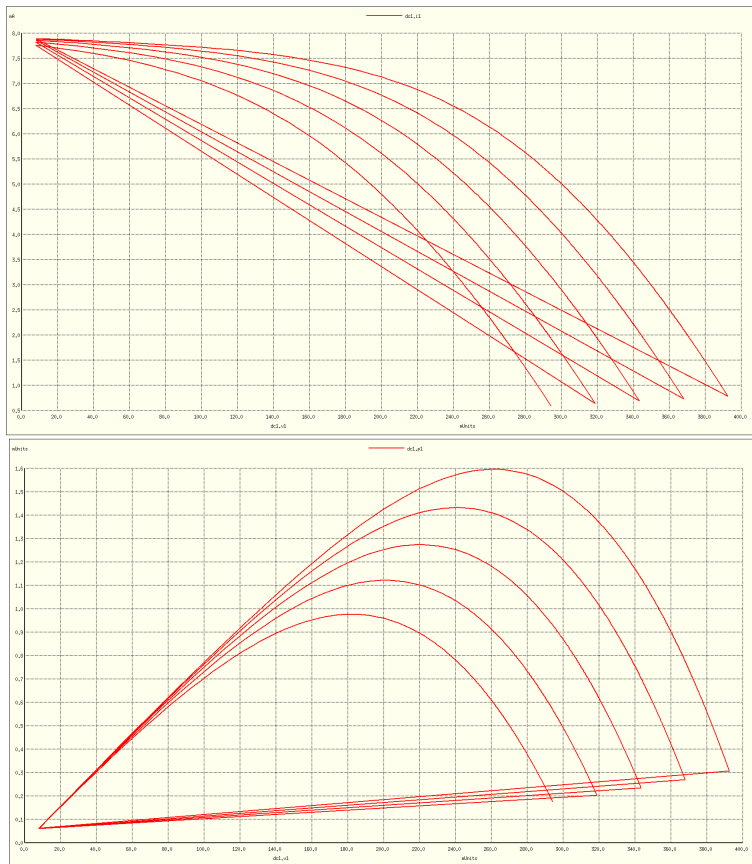


Figure 4:  $I$  vs  $V$  plot and  $P$  vs  $V$  plot

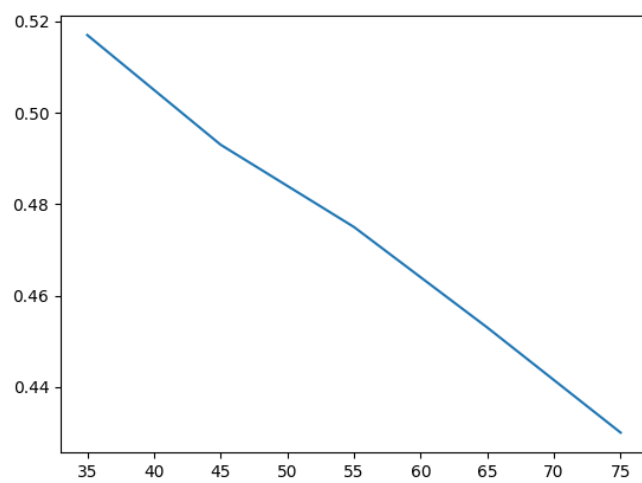


Figure 5: Fill Factor vs Temperature

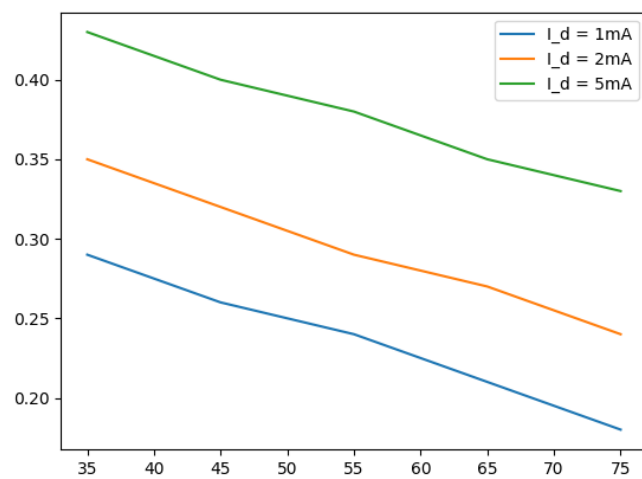


Figure 6:  $V_d$  vs Temperature



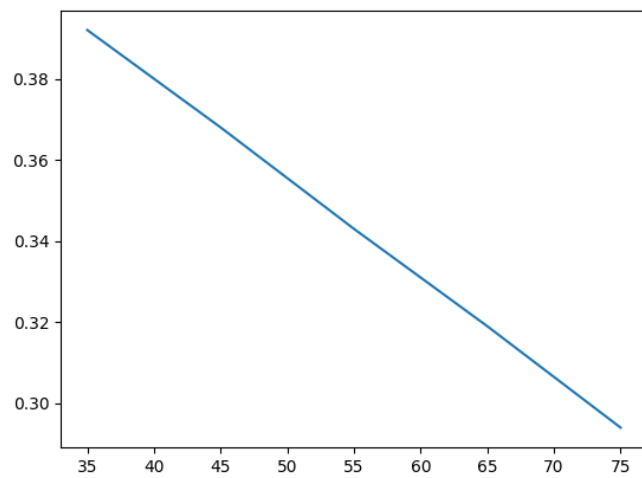


Figure 7:  $V_{oc}$  vs Temperature

### 3 Effect of $R_S$ and $R_{sh}$

Same circuits as that of parts 1 and 2 are used.

Netlist for part A:

```
19D070052 Sheel Shah Solar IV
```

```
.include Solar_Cell.txt
```

```
v_dc 1 0
```

```
r_s1 1 21 100
```

```
x1 21 31 solar_cell IL_val = 8e-3 rsh_val = 100
```

```
v_dummy1 31 0 0
```

```
r_s2 1 22 100
```

```
x2 22 32 solar_cell IL_val = 8e-3 rsh_val = 500
```

```
v_dummy2 32 0 0
```

```
r_s3 1 23 100
```

```
x3 23 33 solar_cell IL_val = 8e-3 rsh_val = 5k
```

```
v_dummy3 33 0 0
```

```
.dc v_dc -2 2 0.01
```

```
* start control
```

```
.control
```

```
set color0 = rgb:f/f/e
```

```
set color1 = rgb:1/1/1
```

```
run
```

```
plot i(v_dummy1) vs v(21)-v(31), i(v_dummy2) vs v(22)-v(32), i(v_dummy3) vs v(23)-v(33)
```

```
* end control
```

```
.endc
```

```
.end
```

Netlist for part B:

```
19D070052 Sheel Shah Solar IV
```

```
.include Solar_Cell.txt
```

```
r1 0 21 100
```

```
x1 21 31 solar_cell IL_val = 8e-3 rsh_val = 100
```

```
v_dummy1 0 31 0
```

```
r2 0 22 100
```

```
x2 22 32 solar_cell IL_val = 8e-3 rsh_val = 500
```

```
v_dummy2 0 32 0
```

```
r3 0 23 100
```

```
x3 23 33 solar_cell IL_val = 8e-3 rsh_val = 5k
```

```
v_dummy3 0 33 0
```

```
* start control
```

```
.control
```

```
set color0 = rgb:f/f/e
```

```
set color1 = rgb:1/1/1
```

```
run
```

```
dc r1 1 500 1
```

```
let i1 = i(v_dummy1)
```

```
let v1 = v(21)-v(31)
```

```
let p1 = i1*v1
```

```
dc r2 1 500 1
```

```
let i2 = i(v_dummy2)
```

```
let v2 = v(22)-v(32)
```

```
let p2 = i2*v2
```

```
dc r3 1 500 1
```

```

let i3 = i(v_dummy3)
let v3 = v(23)-v(33)
let p3 = i3*v3

plot dc1.i1 vs dc1.v1, dc2.i2 vs dc2.v2, dc3.i3 vs dc3.v3
plot dc1.p1 vs dc1.v1, dc2.p2 vs dc2.v2, dc3.p3 vs dc3.v3

** values(rs 0 10 30)
** i_sc = 8m, 7.9m, 7.6m
** v_oc = 0.42, 0.41, 0.39
** p_mp = 2.16m, 1.74m, 1.12m
** ff = 0.64, 0.54, 0.38

** values(rsh 100 500 5k)
** i_sc = 7.2m, 7.8m, 8m
** v_oc = 0.38, 0.41, 0.42
** p_mp = 1.11m, 1.66m, 1.80m
** ff = 0.41, 0.52, 0.54

* end control
.endc

.end

```

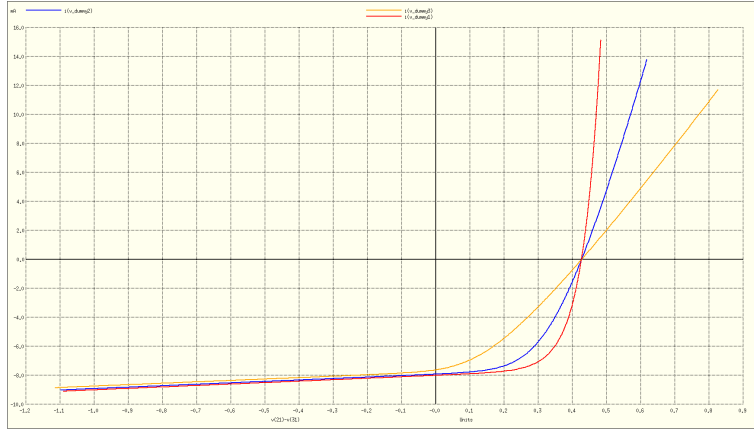


Figure 8: I vs V plot as  $R_s$  changes  
The curve flattens as the series resistance increases.

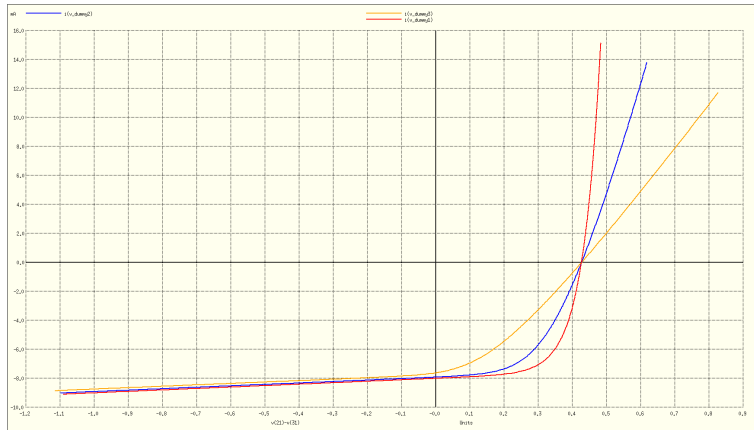


Figure 9: I vs V plot as  $R_{sh}$  changes  
The curve becomes more ideal for high shunt resistance, and  $I_l$  approaches the desired value.

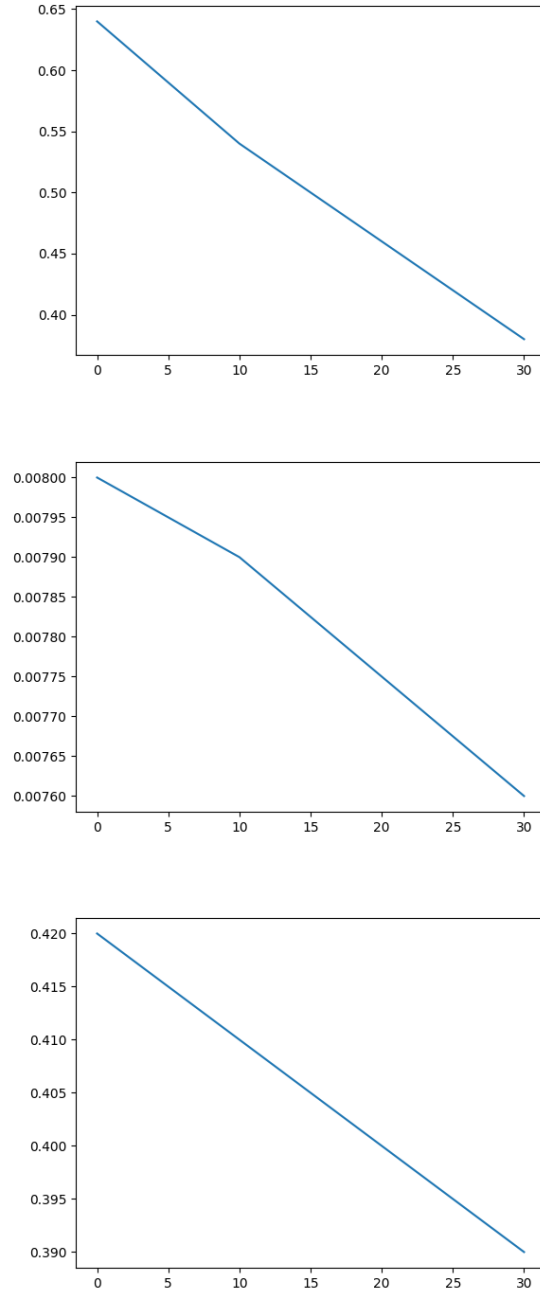


Figure 10: Fill Factor,  $I_{sc}$ ,  $V_{oc}$  vs  $R_s$ , all have a decreasing trend.

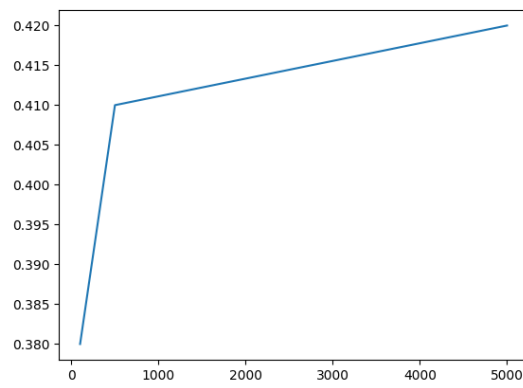
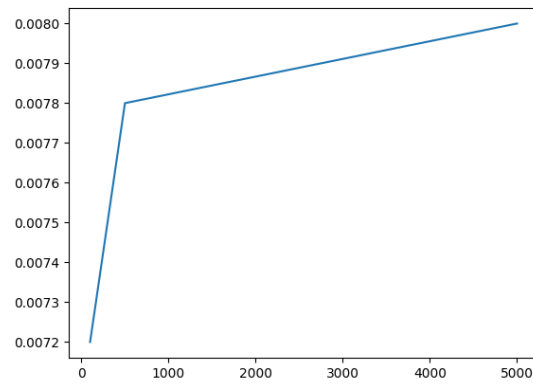
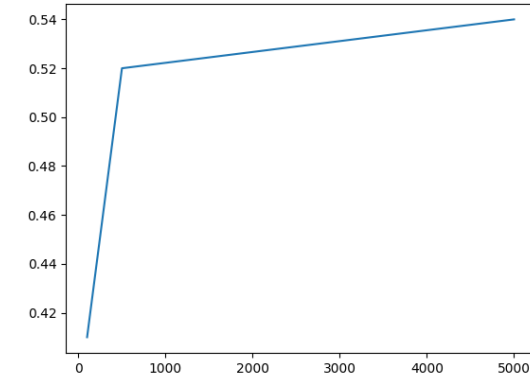


Figure 11: Fill Factor,  $I_{sc}$ ,  $V_{oc}$  vs  $R_{sh}$ , all have a increasing trend.

## 4 Experiment completion status

I was able to complete all parts of the experiment.