

EE236: Experiment 5

Sheel F. Shah, 19D070052

March 9, 2022

Overview of the experiment

0.1 Aim of the experiment

The aim of this experiment was to understand the workings and characteristics of MOSFETs along with non-idealities.

0.2 Report Pattern

Instead of following the template, I have split the report into sections based on the questions/simulations. Each section is based on one question/simulation, and all associated details are in that section only.

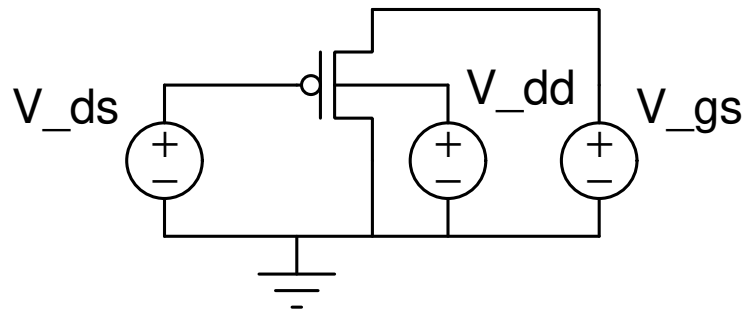


Figure 1: Circuit used. The same circuit has been used for all parts and the values of the voltages have changed, as can be seen in the code

1 $I_d - V_{ds}$ characteristics

Netlist used:

19D070052 Sheel Shah I_d vs V_ds

```
.include pmos.txt
```

```
** 1 2 3 4: drain gate source body
```

```
m1 1 2 0 4 ALD1107
```

```
v_dd 4 0 2
```

```
v_id 10 1 0
```

```
v_ds 10 0
```

```
v_gs 2 0
```

```
.dc v_ds -5 0 0.1 v_gs -4 -2.5 0.5
```

```
* start control
```

```
.control
```

```
set color0 = rgb:f/f/e
```

```
set color1 = rgb:1/1/1
```

```
run
```

```
plot i(v_id) vs v(10)
```

```
** rds by seeing dx/dy near origin:
```

```
** -2.5: 3.8k, -3: 2.9k, -3.5: 2.3k, -4: 1.8k
```

```
** r_0 by seeing dx/dy in saturation:
```

```
** -2.5: 168302, -3: 92307, -3.5: 59446, -4: 40978
```

```
** early voltage:
```

```
** sat dy/dx = 1.70246e-05, x0 = -4.68615, y0 = -0.000619565
```

```
** c = y-mx = -0.000619565 - 1.70246e-05*(-4.68615) = -5.39785e-04
```

```
** v_a = -c/m = 3.170618e+01
```

.endc

.end

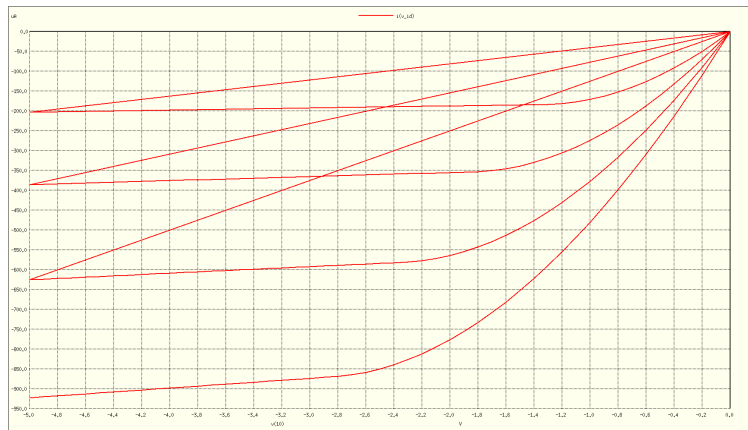


Figure 2: IV Characteristics

Calculation and values of R_{ds} , R_0 , V_A have been mentioned in code

2 V_t and gm measurement

2.1 Linear Region

19D070052 Sheel Shah I_d vs V_ds

```
.include pmos.txt

** 1 2 3 4: drain gate source body
m1 1 2 0 4 ALD1107
v_dd 4 0 0
v_id 10 1 0
v_ds 10 0 -0.2
v_gs 2 0

.dc v_gs -5 0 0.1

* start control
.control
set color0 = rgb:f/f/e
set color1 = rgb:1/1/1

run

plot i(v_id) vs v(2)

** v_t by extrapolating linear region: -0.91
** gm = 4.03441e-05
.endc

.end
```

All measured values are mentioned in the code

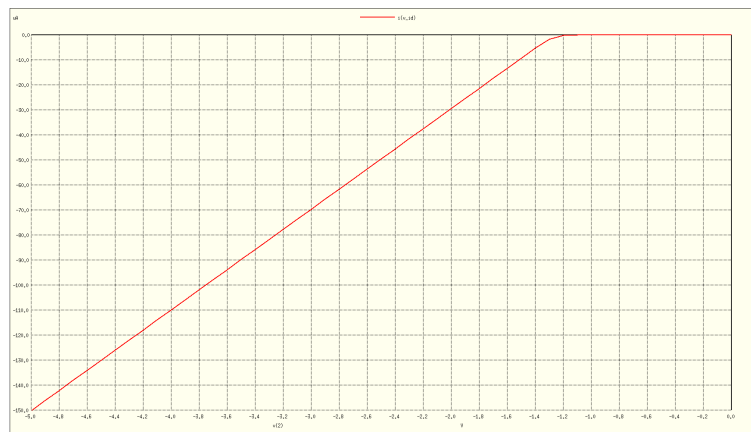


Figure 3: I vs V plot in linear region

2.2 Saturation Region

19D070052 Sheel Shah I_d vs V_{ds}

```
.include pmos.txt

** 1 2 3 4: drain gate source body
m1 1 2 0 4 ALD1107
v_dd 4 0 2
v_id 10 1 0
v_ds 10 0 -5
v_gs 2 0

.dc v_gs -5 0 0.1

* start control
.control
set color0 = rgb:f/f/e
set color1 = rgb:1/1/1

run

plot (i(v_id)) vs v(2)

** vt by linear region's intercept: -1.18
**  $g_m = 2I_d/(v_{ds} - v_t) = 6e-4$ 
**  $K = 2 * \text{slope} * \text{slope} = 2.321322e-04 \text{ A/V}^2$ 
.endc

.end
```

All measured values are mentioned in the code

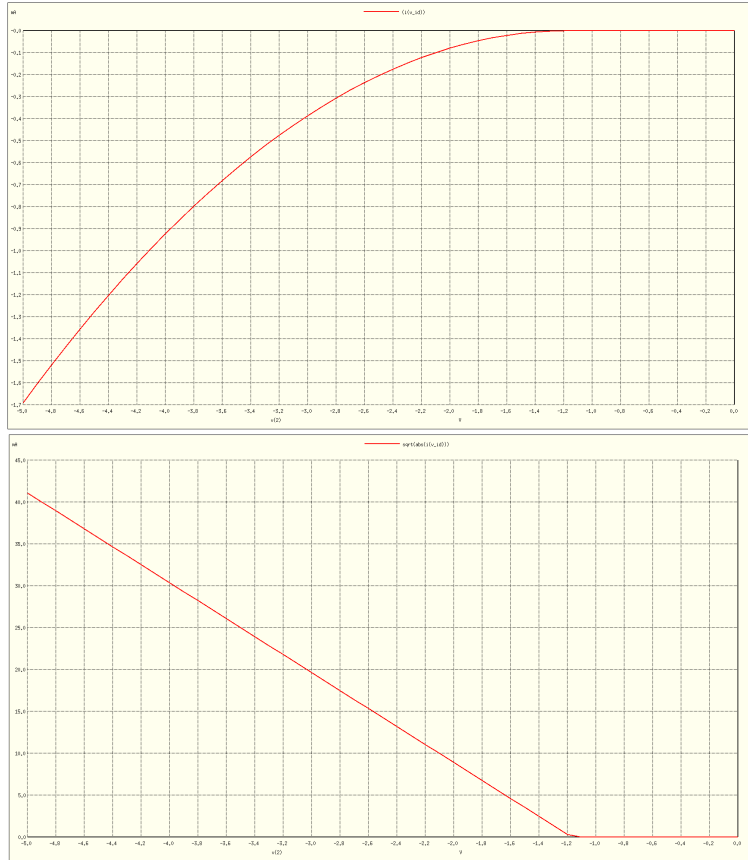


Figure 4: I vs V plot, $\sqrt{|I|}$ vs V plot in saturation region

3 Effect of body bias

19D070052 Sheel Shah I_d vs V_{ds}

```
.include pmos.txt

** 1 2 3 4: drain gate source body
m1 1 2 0 4 ALD1107
v_dd 4 0
v_id 10 1 0
v_ds 10 0 -0.2
v_gs 2 0

.dc v_gs -5 0 0.1 v_dd 0 4 1

* start control
.control
set color0 = rgb:f/f/e
set color1 = rgb:1/1/1

run

plot i(v_id) vs v(2)

** vt by extrapolating linear region:
** 0: -0.9,-1: -1.13, -2: -1.26, -3: -1.36, -4: -1.48
** vt increases in magnitude as vsb increases in magnitude

** -0.9 = vto
** -1.48 = -0.9 + gamma(sqrt(4.8) - sqrt(0.8))
** gamma = -0.447
.endc

.end
```

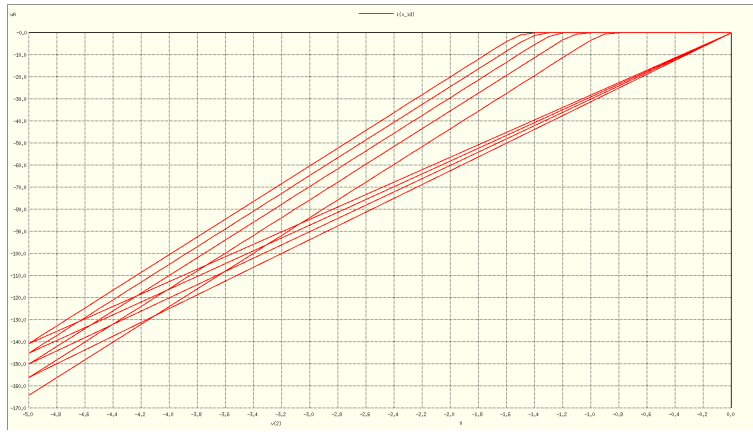


Figure 5: I vs V_{gs} plot as V_{sb} changes
Measurements and calculations are mentioned in the code

4 Experiment completion status

I was able to complete all parts of the experiment.